

## Lab 2: Pre lab

Carson  
Murray

Part 1:

Resistance of Thermistor at 20°C = 12488  $\Omega$

Resistance of Thermistor at 40°C = 5330  $\Omega$

Voltage Divider Equation:

$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

Calculations for Configuration in Figure 3a:

At 20°C:

$V_{in} = 5V$   $R_1 = 12488 \Omega$   $R_2 = 10k\Omega$

$$V_{out} = 5V \cdot \frac{10000 \Omega}{12488 \Omega + 10000 \Omega} = \boxed{2.223 V}$$

At 40°C:

$V_{in} = 5V$   $R_1 = 5330 \Omega$   $R_2 = 10k\Omega$

$$V_{out} = 5V \cdot \frac{10000 \Omega}{5330 \Omega + 10000 \Omega} = \boxed{3.262 V}$$

Calculations for Configuration in figure 3b:

At 20°C:

$V_{in} = 5V$   $R_1 = 10k\Omega$   $R_2 = 12488 \Omega$

$$V_{out} = 5V \cdot \frac{12488 \Omega}{10000 \Omega + 12488 \Omega} = \boxed{2.777 V}$$

At 40°C:

$V_{in} = 5V$   $R_1 = 10k\Omega$   $R_2 = 5330 \Omega$

$$V_{out} = 5V \cdot \frac{5330 \Omega}{10000 \Omega + 5330 \Omega} = \boxed{1.738 V}$$

Part 2:

Resistance Estimate at 10 lux  $\approx 15 \text{ k}\Omega$

Resistance Estimate at 500 lux  $\approx 200 \Omega$

Calculations for Configuration in 3a:

At 10 lux:

$$V_{in} = 5V \quad R_1 = 15000\Omega \quad R_2 = 10000\Omega$$

$$V_{out} = 5V \cdot \frac{10000\Omega}{15000\Omega + 10000\Omega} = \boxed{2V}$$

At 500 lux:

$$V_{in} = 5V \quad R_1 = 200\Omega \quad R_2 = 10000\Omega$$

$$V_{out} = 5V \cdot \frac{10000\Omega}{200\Omega + 10000\Omega} = \boxed{4.982V}$$

Calculations for Configuration in 3b:

at 10 lux:

$$V_{in} = 5V \quad R_1 = 10000\Omega \quad R_2 = 15000\Omega$$

$$V_{out} = 5V \cdot \frac{15000\Omega}{10000\Omega + 15000\Omega} = \boxed{3V}$$

At 500 lux:

$$V_{in} = 5V \quad R_1 = 200\Omega \quad R_2 = 10000\Omega$$

$$V_{out} = 5V \cdot \frac{200\Omega}{10000\Omega + 200\Omega} = \boxed{0.098V}$$