

Lab 3 Prelab

Colson
Murray

Part 1:

Current ranges from 100-300 mA when 10V is applied.

Ohm's Law: $V = IR$

Assuming the Motor is drawing 200 mA, I believe a resistor with $3\ \Omega$ should be used as the measuring resistor.

$$V = 0.200\text{A} \cdot 3\ \Omega = 0.6\text{V}$$

I chose 200 mA as the current draw because it is in the middle range of possible current draw, but the $3\ \Omega$ resistor performs well at the lowest and highest possible current as well.

$$\text{at } 100\text{mA: } 0.100\text{A} \cdot 3\ \Omega = 0.3\text{V}$$

$$\text{at } 300\text{mA: } 0.300\text{A} \cdot 3\ \Omega = 0.9\text{V}$$

at the lowest voltage, the oscilloscope would still be able to read it, and at the highest current, the voltage across the resistor is less than 10% of the input voltage (10V)

Formula for Power: $P = I^2 R$

Power dissipated across the highest current:

$$P = (0.300\text{A})^2 \cdot 3\ \Omega = 0.27\text{W}$$

The power rating for this resistor is $\frac{1}{2}\text{W}$.